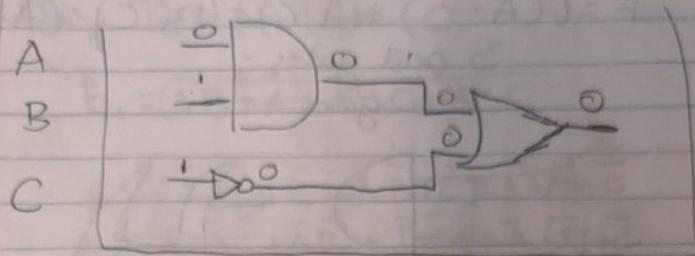


Javier Escareno CSC113



2.

x_2	x_1	x_0	F_1	\bar{F}_2	\bar{F}_3	F_4
0	0	0	0	0	1	0
0	0	1	0	1	1	0
0	1	0	0	1	1	0
0	1	1	1	0	0	0
1	0	0	0	1	0	1
1	0	1	1	0	0	1
1	1	0	1	0	0	1
1	1	1	0	1	0	1

$$F_1 = (\bar{x}_2 \cdot x_1 \cdot x_0) + (x_2 \cdot \bar{x}_1 \cdot x_0) + (x_2 \cdot x_1 \cdot \bar{x}_0)$$


$$F_2 = (\bar{x}_2 \cdot \bar{x}_1 \cdot x_0) + (\bar{x}_2 \cdot x_1 \cdot \bar{x}_0) + (x_1 \cdot \bar{x}_2 \cdot \bar{x}_0) + (\bar{x}_2 \cdot x_1 \cdot \bar{x})$$

$$F_3 = (\bar{x}_2 \cdot \bar{x}_1 \cdot \bar{x}_0) + (\bar{x}_2 \cdot \bar{x}_1 \cdot x_0) + (\bar{x}_2 \cdot x_1 \cdot \bar{x}_0) + (\bar{x}_2 \cdot x_1 \cdot x_0)$$


$$F_4 = (x_2 \cdot \bar{x}_1 \cdot \bar{x}_0) + (x_2 \cdot \bar{x}_1 \cdot x_0) + (x_2 \cdot x_1 \cdot \bar{x}_0) + (x_2 \cdot x_1 \cdot x_0)$$

3. $F = ((A \cdot B) + (A \cdot C)) + (B \cdot C) \cdot (A \cdot B \cdot C)$

3 and gates
2 or gates +

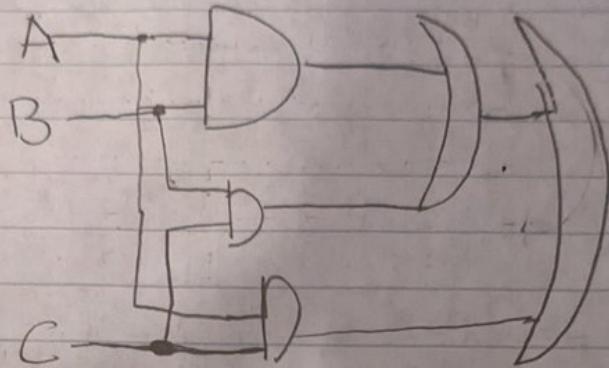
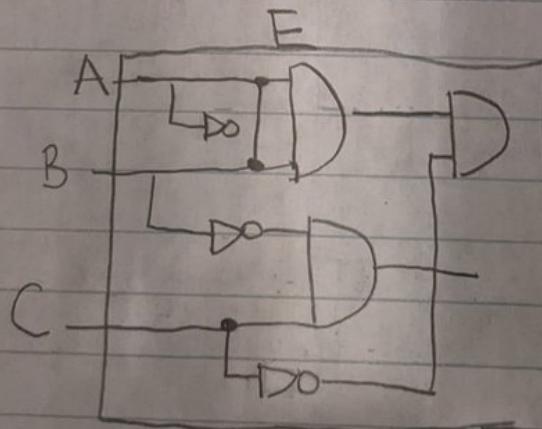
$$F = (A \cdot B \cdot C) + (A \cdot \bar{B} \cdot C) + (\bar{A} \cdot B \cdot C)$$



Reasoning: When it comes to which gate is much more efficient it would be the first equation. The reason for it is because the first equation only has 5 gates while the second gate has 6

4 Using DeMorgan's Law:

$$E_1 = \overline{(AB + AC + BC)} \cdot ABC$$

$$\begin{aligned} E_1 &= (\bar{A} + \bar{B})(\bar{A} + \bar{C})(\bar{B} + \bar{C}) + \bar{A} + \bar{B} + \bar{C} \\ &= (\bar{A} + \bar{A}\bar{C} + \bar{A}\bar{B} + \bar{B}\bar{C}) + \bar{A} + \bar{B} + \bar{C} \\ &= \bar{A}[1 + \bar{C} + \bar{B}] + \bar{B}\bar{C}(\bar{B} + \bar{C}) + \bar{A} + \bar{B} + \bar{C} \\ &= (\bar{A} + \bar{B}\bar{C})(\bar{B} + \bar{C}) + \bar{A} + \bar{B} + \bar{C} \\ &= \bar{A}\bar{B} + \bar{B}\bar{C} + \bar{A}\bar{C} + \bar{B}\bar{C} + \bar{A} + \bar{B} + \bar{C} \\ &= A[1 + \bar{B} + \bar{C}] + \bar{B}[1 + \bar{C}] + \bar{C} \\ &= \bar{A} + \bar{B} + \bar{C} \\ E_1 &= \bar{ABC} \end{aligned}$$

$$E_2 = \overline{\bar{ABC} + \bar{ABC} + ABC}$$

$$\begin{aligned} &= (\bar{A} + \bar{B} + \bar{C})(\bar{A} + \bar{B} + \bar{C})(\bar{A} + \bar{B} + \bar{C}) \\ &\quad \overline{x \cdot x' \cdot x} = \bar{x} \\ \bar{A} + \bar{B} + \bar{C} &= \boxed{\bar{ABC} = E_2} \end{aligned}$$


S.) Xor₁ = $(A \cdot \bar{B}) + (\bar{A} \cdot B)$

$$(A + \bar{B}) \cdot (\bar{A} + B)$$

$$\begin{aligned} X_{\text{or}_2} &= (\bar{A} + \bar{B})AB = A \cdot \bar{A} + A\bar{B} + B\bar{B} + \bar{A}B \\ A \cdot \bar{A} &= 0, \bar{B} \cdot B = 0 = A\bar{B} + \bar{A}B \end{aligned}$$

(6.)

A	B	C	Xor
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

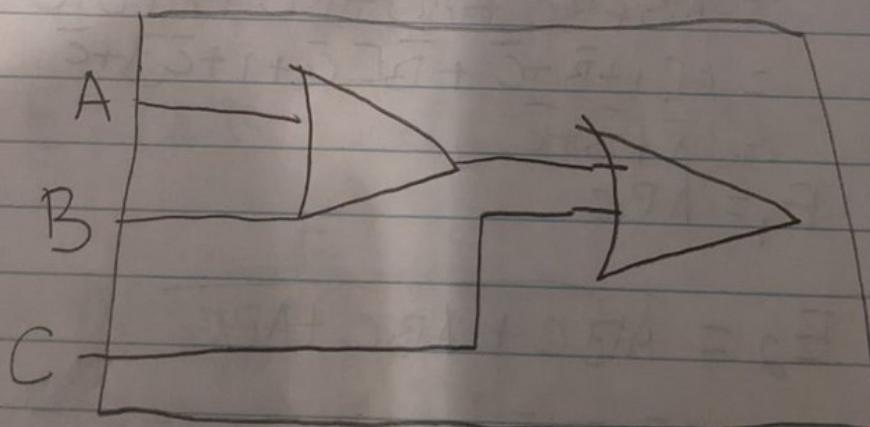

$$\begin{aligned} \text{Xor} = & (\bar{A} \cdot \bar{B} \cdot C) + (\bar{A} \cdot B \cdot \bar{C}) + (A + \bar{B} \cdot C) \\ & + (A \cdot B \cdot C) \end{aligned}$$